

Exercise 1 :

1. Establish the truth tables for the following functions:

✓ $F1 = (X + Y)(\bar{X} + Y + Z)$

✓ $F2 = (\bar{X}Y + X\bar{Y})\bar{Z} + (\bar{X}\bar{Y} + XY)Z$

2. Demonstrate the following equivalences using truth tables:

$X + YZ = (X+Y)(X+Z)$

$(\bar{X} + Y)(X + Z)(Y + Z) = (\bar{X} + Y)(X + Z)$

Exercise 2 :

1. Simplify the following expressions algebraically:

✓ $(x + \bar{y} + x \bar{y})(xy + \bar{x}z + yz)$

✓ $(x + y + z)(\bar{x} + y + z) + xy + yz$

✓ $abcd + abchg + \bar{d}hg + abcdefh.$

✓ $a\bar{c}de + \bar{d} + \bar{e} + c$

2. Prove the following equality algebraically:

✓ $A\bar{B} + \bar{A}\bar{C}\bar{D} + \bar{A}\bar{B}D + \bar{A}\bar{B}C\bar{D} = \bar{A}\bar{C}\bar{D} + \bar{B}$

✓ $A.B + \bar{A}.C + B.C = A.B + \bar{A}.C$

✓ $AB + ACD + \bar{B}D = AB + \bar{B}D$

✓ $AB + \bar{B}C = (A + \bar{B})(B + C)$

Exercise 3 :


Simplify using De Morgan's theorem:

$S = \overline{(x + \bar{y} + \bar{z})(x + \bar{\bar{y}}\bar{\bar{z}})} + \bar{x}\bar{y}(\bar{z}t + tz)$

$T = \overline{\overline{(a\bar{b})(b+c+\bar{d})} + bc}$

Exercise 4 :

1. Draw up the truth table for the circuit below.
2. Extract the equation of S from the truth table.

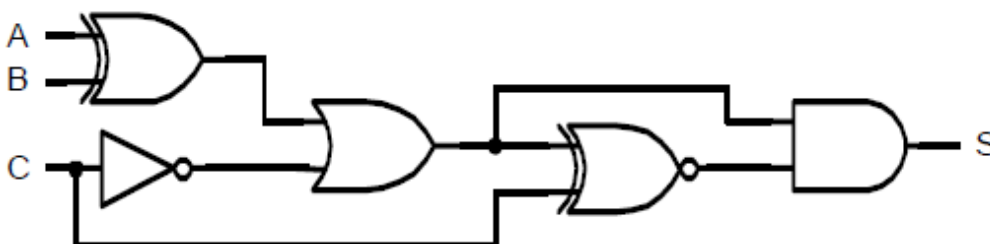

Exercise 5 :

Simplify the functions given by the Karnaugh maps. Create circuits using only NAND gates, then only NOR gates:

ab\cd	00	01	11	10
00	1	1	1	
01		1	1	
11		1	1	
10	1	1	1	1

ab\cd	00	01	11	10
00	1			1
01		1	1	
11		1	1	
10	1			1

ab\cd	00	01	11	10
00	1			1
01	1	1		1
11		1	1	
10	1		1	1

ab\cd	00	01	11	10
00		X	X	1
01		1	1	1
11		1	1	
10		1	1	

ab\cd	00	01	11	10
00	1			1
01	X	1	1	1
11	X	1	1	X
10	X			

ab\cd	00	01	11	10
00	1	1		1
01	1	1	X	1
11	1	1		1
10	X	X		

Exercise 6 :

Use the Karnaugh maps to simplify the following functions, then create the corresponding circuits using NOR or NAND gates.

$F(a, b, c) = \Pi(0, 1, 2, 3, 4, 7)$

$G(a, b, c, d) = \Sigma(2, 6, 7, 10, 11, 12, 14)$


Exercise 7 :

1. Let F be a function consisting only of NOR functions:

$$F = \overline{\overline{(x + y + z)} + (\overline{x + y + \overline{z}}) + \overline{x} + y + z}$$

Give the truth table, the first canonical form and the corresponding function composed only of NAND.

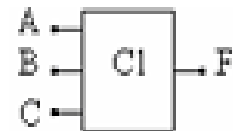2. Let F(A,B,C) be a function defined as follows:



- $F(A,B,C) = 1$ if $(ABC)_2$ contains an odd number of 1's;
- $F(A,B,C) = 0$ else.

- a) Establish the truth table for F.
- b) Give the algebraic equation of F.
- c) Draw the C1 circuit diagram of function F with the minimum number of logic gates.